

Phys 112 HWS Garrett Haldrop

No.

Date

Q: 1, 2, 5, 6, 7 P: 1, 3, 4, 9, 14, 15, 19, 20, 32, 42, 49

Qs

1: $q = C\Delta V$ $C = \frac{\epsilon_0 A}{d}$ C_1 $q = \frac{\epsilon_0 A \Delta V}{d}$ C_2 $q = \frac{\epsilon_0 2A \Delta V}{d}$ C_3 $q = \frac{\epsilon_0 A \Delta V}{2d}$

$\boxed{\text{plot a} = C_2 \text{ plot b} = C_1 \text{ plot c} = C_3}$

2: a) Series $\frac{1}{C_{eq}} = \frac{1}{C_1} + \frac{1}{C_2} + \frac{1}{C_3}$ b) Parallel $C_{eq} = C_1 + C_2 + C_3$

c) There is more charge on the capacitors in parallel

5: a) The potential difference across C_1 remains the same

b) The charge across C_1 remains the same.

c) The capacitance of C_{12} is more than C_1 $C_{eq} = C_1 + C_2$

d) The charges stored on C_1 and C_2 is more than C_1

6: a) The potential difference across C_1 is lower.

b) The charge across C_1 remains the same

c) The capacitance of C_{12} is less than C_1 $\frac{1}{C_{eq}} = \frac{1}{C_1} + \frac{1}{C_2}$

d) The charge stored on C_1 and C_2 is the same as C_1

7: a) Series b) Parallel c) Parallel

Ps

1: a) $C = \frac{q}{V}$ $q = 70 \text{ pC}$ $\Delta V = 20 \text{ V}$ $C = \frac{70 \text{ pC}}{20 \text{ V}} = 3.5 \text{ pF}$

b) stays the same because based off $\frac{\epsilon_0 A}{d}$ so 3.5 pF

c) $V = \frac{q}{C}$ $q = 200 \text{ pC}$ $C = 3.5 \text{ pF}$ $V = \frac{200 \text{ pC}}{3.5 \text{ pF}} = 57.1 \text{ V}$

3: a) $r = 8.2 \text{ cm}$ $d = 1.3 \text{ mm}$ $A = \pi r^2 = \pi (8.2 \text{ cm})^2 = 0.02 \text{ m}^2$

$\boxed{C = \frac{\epsilon_0 \cdot 0.02 \text{ m}^2}{1.3 \text{ mm}} = 143.8 \text{ pF}}$

b) $q = C\Delta V$ $\Delta V = 120 \text{ V}$ $q = 143.8 \text{ pF} \cdot 120 \text{ V} = \boxed{17.3 \text{ nC}}$

4: $r_1 = 38 \text{ mm}$ $r_2 = 40 \text{ mm}$ $C = 4\pi\epsilon_0 \frac{r_1 r_2}{r_2 - r_1}$

$C = 4\pi\epsilon_0 \frac{38 \text{ mm} \cdot 40 \text{ mm}}{40 \text{ mm} - 38 \text{ mm}} = \boxed{84.5 \text{ pF (a)}}$

b) $d = 2 \text{ mm}$ $C = \frac{\epsilon_0 A}{d}$ $A = \frac{Cd}{\epsilon_0} = \frac{84.5 \text{ pF} \cdot 2 \text{ mm}}{\epsilon_0} = 191 \text{ cm}^2$

9: $C_{1,2} = 25 \text{ pF}$ $C_{eq} = C_1 + C_2 + C_3 = 75 \text{ pF}$ $V = 4200 \text{ V}$

$q = CV = 75 \text{ pF} \cdot 4200 \text{ V} = \boxed{0.315 \text{ C}}$

Garrett Holdings

14: all $C = 10 \mu F$ $V = 10V$ $C_{eq} = C_1 + C_{2345}$ $C_{2345} = \frac{1}{C_{234}} + \frac{1}{C_5}$ $C_{234} = C_{23} + C_4$

$C_{23} = \frac{1}{\frac{1}{10 \mu F} + \frac{1}{10 \mu F}} = 5 \mu F$ $C_{234} = 5 \mu F + 10 \mu F = 15 \mu F$

$\frac{1}{C_{23}} = \frac{1}{C_2} + \frac{1}{C_3}$

$C_{2345} = \frac{1}{\frac{1}{15 \mu F} + \frac{1}{10 \mu F}} = 6 \mu F$ $C_{eq} = 10 \mu F + 6 \mu F = 16 \mu F$ $q_{eq} = CV = 16 \mu F \times 10V = 160 \mu C$

$q_{eq} = q_1 + q_{2345}$ $q_1 = C_1 V = 10 \mu F \cdot 10V = 100 \mu C$


b) $q_{2345} = q_{eq} - q_1 = 160 \mu C - 100 \mu C = 60 \mu C$ $q_{2345} = q_{234} = q_5$ $q_{234} = 60 \mu C$

$V_{234} = \frac{q_{234}}{C_{234}} = \frac{60 \mu C}{15 \mu F} = 4V$ $q_{23} = q_{234} - q_4 = 60 \mu C - 40 \mu C = 20 \mu C$ $q_{23} = C_{23} \cdot V_{234} = 10 \mu F \cdot 4V = 40 \mu C$

$q_2 = q_{23} = q_3$

$q_2 = 20 \mu C$

15:

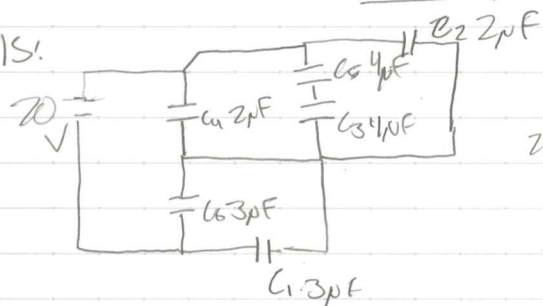

$C_{eq} = \frac{1}{\frac{1}{C_{2345}} + \frac{1}{C_2}}$

$C_{16} = C_1 + C_6$

$C_{2345} = C_4 + C_{35} + C_2$

$C_{35} = \frac{1}{\frac{1}{C_3} + \frac{1}{C_5}}$

$C_{35} = \frac{1}{\frac{1}{4 \mu F} + \frac{1}{4 \mu F}} = 2 \mu F$ $C_{16} = 3 \mu F + 3 \mu F = 6 \mu F$

$C_{2345} = 2 \mu F + 2 \mu F + 2 \mu F = 6 \mu F$

$C_{eq} = \frac{1}{\frac{1}{6 \mu F} + \frac{1}{6 \mu F}} = 3 \mu F$ $q_{eq} = C_{eq} V = 3 \mu F \cdot 20V = 60 \mu C$

a: $C_{eq} = 3 \mu F$
b: $q_{eq} = 60 \mu C$

$q_{eq} = q_{2345} = q_{16}$ $q_{16} = q_1 + q_6$ $V_1 = \frac{q_1}{C_1}$ $q_1 = q_6$

$q_1 = \frac{q_{16}}{2} = \frac{60 \mu C}{2} = 30 \mu C$ $V_1 = \frac{30 \mu C}{3 \mu F} = 10V$

c: $10V$
d: $30 \mu C$

$q_{2345} = q_4 + q_{35} + q_2$

$q_2 = q_{35} = q_4$

$q_2 = \frac{q_{2345}}{3} = \frac{60 \mu C}{3} = 20 \mu C$ $V_2 = \frac{20 \mu C}{2 \mu F} = 10V$

$V_2 = \frac{q_2}{C_2}$

e: $10V$
f: $20 \mu C$


$q_{35} = q_3 = q_5 = q_2$

$V_3 = \frac{q_3}{C_3} = \frac{20 \mu C}{4 \mu F} = 5V$

$q_3 = 20 \mu C$

g: $5V$
h: $20 \mu C$

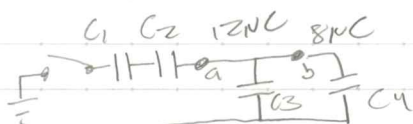19) $V = 9V$ $C_2 = 3\mu F$ $C_4 = 4\mu F$



$$C_{eq} = \frac{1}{\frac{1}{C_2} + \frac{1}{C_4}} \quad C_{12} = \frac{1}{\frac{1}{C_1} + \frac{1}{C_2}} \quad C_{34} = C_3 + C_4$$

$$V_2 = \frac{q_2}{C_2} = \frac{12\mu C}{3\mu C} = 4V \quad V_{eq} = V_{12} + V_{34} \quad V_3 = V_4 \quad V_4 = \frac{q_4}{C_4} = \frac{8\mu C}{4\mu F} = 2V$$

$$V_1 = V_{12} - V_2 = 7V - 4V = 3V \quad V_{12} = 9V - 2V = 7V$$

$$a) \quad C_1 = \frac{q_1}{V_1} = \frac{12\mu C}{3V} = 4\mu F$$

$$b) \quad C_3 = \frac{q_3 - q_4}{V_3} = \frac{12\mu C - 8\mu C}{2V} = 2\mu F$$

20) $C = \frac{\epsilon_0 A}{d}$ $A = 1.25 \text{ cm}^2$ $d = 3.4 \text{ mm}$ $n = 8$ total $C = n - 1 = 7$

$$C_{\text{tot}} = 7\epsilon_0 \cdot \frac{A}{d} = 7\epsilon_0 \cdot \frac{1.25 \text{ cm}^2}{3.4 \text{ mm}} = \boxed{2.28 \text{ pF}}$$

32) $A = 40 \text{ cm}^2$ $d = 1 \text{ mm}$ $\Delta V = 600V$

$$a) \quad C = \frac{\epsilon_0 A}{d} = \frac{\epsilon_0 40 \text{ cm}^2}{1 \text{ mm}} = \boxed{35.4 \text{ pF}} \quad b) \quad q = CV = 35.4 \text{ pF} \cdot 600V = \boxed{21.2 \text{ nC}}$$

$$c) \quad U = \frac{1}{2} CV^2 = \frac{1}{2} 35.4 \text{ pF} \cdot 600V^2 = \boxed{6.37 \text{ nJ}}$$

$$E = \frac{V}{d} = \frac{600V}{1 \text{ mm}} = \boxed{600 \text{ kN/C}} \quad U_E = \frac{1}{2} \epsilon_0 E^2 = \frac{1}{2} \epsilon_0 600 \text{ kN/C}^2 = \boxed{1.59 \text{ J/m}^3}$$

42) a) $C = 50 \text{ pF}$ $A = 0.35 \text{ cm}^2$

b) $k = 5.6$

$$C_n = kC_0 = 5.6 \cdot 50 \text{ pF} = \boxed{280 \text{ pF}}$$

$$c) \quad C = \frac{\epsilon_0 A}{d} \quad d = \frac{\epsilon_0 A}{C} = \epsilon_0 \frac{0.35 \text{ cm}^2}{50 \text{ pF}} = \boxed{6.2 \text{ cm}}$$

49) $A = 7.89 \text{ cm}^2$ $d = 4.62 \text{ mm}$ $k_1 = 11$ $k_2 = 12$

$$C_0 = \frac{\epsilon_0 A}{d/2} = \frac{\epsilon_0 7.89 \text{ cm}^2}{4.62 \text{ mm}/2} = 3.02 \text{ pF}$$

$$C_1 = k_1 C_0 \quad C_2 = k_2 C_0 \quad C_{eq} = \frac{1}{\frac{1}{C_1} + \frac{1}{C_2}}$$

$$C_1 = 11 \cdot 3.02 \text{ pF} = 33.3 \text{ pF} \quad C_2 = 12 \cdot 3.02 \text{ pF} = 36.3 \text{ pF}$$

$$C_{eq} = \frac{1}{\frac{1}{33.3 \text{ pF}} + \frac{1}{36.3 \text{ pF}}} = \boxed{17.4 \text{ pF}}$$