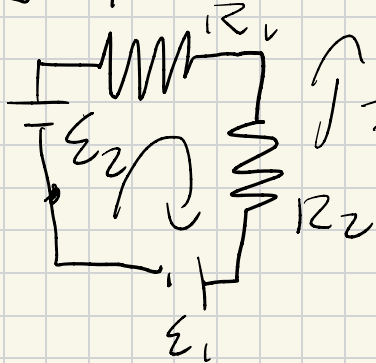


HW > Garrett+HalDrop Ch 27

PS: 1, 3, 12, 16, 18, 22, 29, 33, 58, 64

1) $\mathcal{E}_1 = 12V$ $\mathcal{E}_2 = 6V$ $R_1 = 4\Omega$ $R_2 = 8\Omega$



$$\mathcal{E}_2 - I R_1 - I R_2 - \mathcal{E}_1 = 0$$

$$I R_{eq}$$

$$R_{eq} = R_1 + R_2$$

$$= 4\Omega + 8\Omega \quad 6V - 12\Omega I - 12V = 0$$

$$R_{eq} = 12\Omega$$

$$-12\Omega I = 6V$$

$$P = I^2 R$$

$$I = -0.5A$$

$$P_1 = I^2 R_1 \quad P_2 = I^2 R_2$$

$$P_1 = 0.5^2 \cdot 4\Omega \quad P_2 = 0.5^2 \cdot 8\Omega$$

$$P_1 = 1W$$

$$P_2 = 2W$$

$$P = IV \quad P_{V1} = 0.5A \cdot 12V$$

$$P_{V2} = I \cdot \mathcal{E}_2$$

$$P_{V1} = 6W$$

$$= 0.5A \cdot 6V$$

$$P_{V2} = 3W$$

a) 0.5A

b) 1W

c) 2W

d) 6W

e) 3W

f) supplied

g) absorbed

$$3) \mathcal{E} = 12V \quad R = 0.04\Omega \quad I = 50A$$

$$\Delta V = \mathcal{E} - IR$$

$$= 12V - 0.04\Omega \cdot 50A$$

$$= 12V + 2V$$

$$= 14V$$

$$P_r = V_r \cdot I$$

$$P_r = 2 \cdot 50A$$

$$P_r = 100W$$

$$V_r = RI$$

$$V_r = 0.04 \cdot 50$$

$$V_r = 2$$

$$P_{emf} = \mathcal{E} \cdot I$$

$$= 12V \cdot 50$$

$$= 600W$$

✓ being charged

$$a) 14V$$

$$b) 100W$$

$$c) 600W$$

$$d) 10V$$

$$e) 100W$$

discharging

$$\Delta V = \mathcal{E} - V_r \quad P_r = V_r \cdot I$$

$$= 12V - 2V \quad P_r = 100W$$

$$\Delta V = 10V$$

$$12) R = 6\Omega \quad \mathcal{E} = 12V \quad n = 2 \quad l = 20cm \quad r = 1mm \quad \rho_{copper} = 1.69 \times 10^{-8} \Omega m$$

$$A = \pi r^2$$

$$R_{w1} = \rho \frac{l}{A}$$

$$R_{w1} = 1.69e-8 \cdot \frac{20cm}{3.14 \mu m^2} = 3.14 \mu m^2$$

$$R_{w1} = 1.08 m\Omega$$

$$R_{w1} = R_{w2}$$

$$R_{eq} = R_{w1} + R + R_{w2}$$

$$= 1.08 m\Omega + 6\Omega + 1.08 m\Omega$$

$$R_{eq} = 6.002 \Omega$$

$$P_R = I^2 R \quad P_R = 1.999^2 \cdot 6\Omega$$

$$P_R = 23.98W$$

$$I = \frac{\mathcal{E}}{R}$$

$$= \frac{12V}{6.002\Omega}$$

$$I = 1.999A$$

$$P_w = I^2 \cdot R_{w1} = 1.999 \cdot 1.08 m\Omega = 4.3 mW$$

$$\Delta V_{w1} = I R_{w1}$$

$$= 1.999A \cdot 1.08 m\Omega$$

$$\Delta V_{w1} = 2.15 mV$$

$$\Delta V_{w1} = \Delta V_{w2}$$

$$\Delta V_R = IR$$

$$= 1.999A \cdot 6\Omega$$

$$\Delta V_R = 11.996V$$

$$a) 11.996V \quad b) 2.15 mV$$

$$c) 23.98W \quad d) 4.3 mW$$

$$16) \Delta V_1 = 0.1V \quad R_1 = 500\Omega$$

$$\Delta V_2 = 0.15V \quad R_2 = 1000\Omega$$

$$A = 5\text{cm}^2 \quad \text{Power Rate} = 2\text{mW/cm}^2$$

$$P_{in} = A \cdot \text{Power Rate}$$

$$= 5\text{cm}^2 \cdot 2\text{mW/cm}^2$$

$$P_{in} = 10\text{mW}$$

$$I_1 = \frac{\Delta V_1}{R_1} = \frac{0.1V}{500\Omega} = 0.2\text{mA}$$

$$I_2 = \frac{\Delta V_2}{R_2} = \frac{0.15V}{1000\Omega} = 0.15\text{mA}$$

$$P_{out} = \frac{V^2}{R} = \frac{0.15^2}{1000} = 0.0225\text{mW}$$

$$\mathcal{E} - I_1 r = \Delta V_1 \quad \mathcal{E} - I_2 r = \Delta V_2 \quad \text{eff} = \frac{P_{out}}{P_{in}} \times 100$$

$$\mathcal{E} = \Delta V_1 + I_1 r \quad \mathcal{E} = \Delta V_2 + I_2 r$$

$$= \frac{0.0225\text{mW}}{10\text{mW}} \times 100$$

$$\Delta V_1 + I_1 r = \Delta V_2 + I_2 r$$

$$0.1V + 0.2r = 0.15 + 0.15r$$

$$0.2r = 0.05V + 0.15r$$

$$0.05\text{mA}r = 0.05V$$

$$r = 1000\Omega$$


$$\text{eff} = 0.225\%$$

- a) 1000Ω
b) 0.3V
c) 0.225%

$$\mathcal{E} = \Delta V_1 + I_1 r$$

$$= 0.1V + 0.2\text{mA} \cdot 1000\Omega$$

$$= 0.3V$$

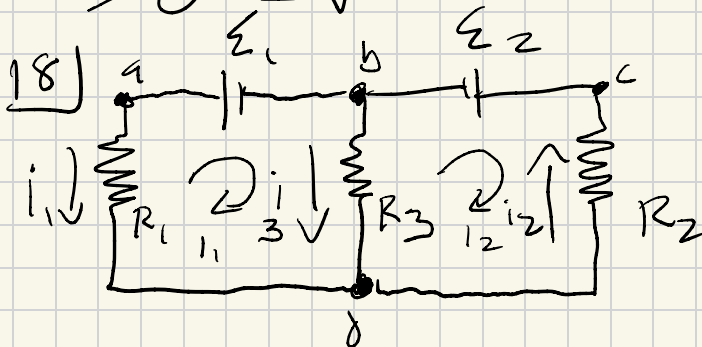

$$\mathcal{E}_1 = 4V \quad \mathcal{E}_2 = 1V \quad V_{bc} = V_{R2}$$

$$R_1 = R_2 = 10\Omega$$

$$R_3 = 5\Omega$$

$$V_{R2} = I_2 \cdot R_2$$

$$= 0.0025A \cdot 10\Omega$$

$$V_{R2} = 0.25V$$

$$i_1 + i_3 = i_2$$

$$1) -\mathcal{E}_1 - i_3 R_3 + i_1 R_1 = 0 \quad 0.275A + -0.25A = i_2$$

$$i_2 = 0.0025A$$

$$2) \mathcal{E}_2 + i_2 R_2 + i_3 R_3 = 0$$

$$\mathcal{E}_2 + (i_1 + i_3) R_2 + i_3 R_3 = 0 \quad -\mathcal{E}_1 - \left(\frac{-\mathcal{E}_2 - i_1 R_2}{R_2 + R_3} \right) R_3 + i_1 R_1 = 0$$

$$\mathcal{E}_2 + i_1 R_2 + i_3 R_2 + i_3 R_3 = 0 \quad -4V - \left(\frac{-1V - i_1 10\Omega}{15\Omega} \right) 5\Omega + i_1 10\Omega = 0$$

$$i_3 = \frac{-\mathcal{E}_2 - i_1 R_2}{R_2 + R_3}$$

$$= \frac{-1V - 0.275A \cdot 10\Omega}{15\Omega}$$

$$i_3 = -0.25A$$


$$-4V + \frac{1}{3}V + i_1 \frac{10}{3}\Omega + i_1 10\Omega = 0$$

$$i_1 = \frac{11}{40}A = 0.275A \quad \frac{40}{3}\Omega = \frac{11}{3}V$$


$$\Delta V_{bc} = 0.25V$$

22)

$$R = 5 \Omega$$

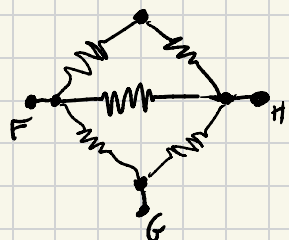

1) F to H

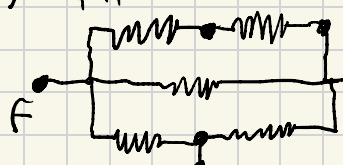

$$R_{eq} = 1.5 \Omega$$


$$\frac{1}{R_{eq}} = \frac{1}{R_{12}} + \frac{1}{R_3} + \frac{1}{R_{45}}$$

$$\frac{1}{R_{12}} = \frac{1}{R_{45}} = \frac{1}{R_1} + \frac{1}{R_2} = \frac{1}{5} + \frac{1}{5} = \frac{2}{5}$$

$$R_{12} = 2.5 \Omega$$

$$\frac{1}{R_{eq}} = \frac{1}{2.5 \Omega} + \frac{1}{5 \Omega} + \frac{1}{2.5 \Omega} = \frac{1}{1.5 \Omega}$$

2) F to G

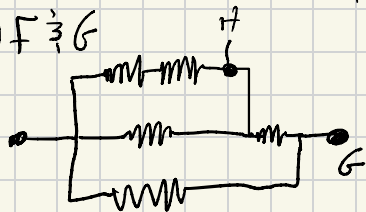

$$\frac{1}{R_{eq}} = \frac{1}{R_{1234}} + \frac{1}{R_5} \quad R_{12} = 10 \Omega$$

$$R_{1234} = R_{123} + R_4 \quad \frac{1}{R_{23}} = \frac{1}{10} + \frac{1}{5} = \frac{3}{10}$$


$$\frac{1}{R_{23}} = \frac{1}{R_2} + \frac{1}{R_3} \quad R_{23} = \frac{10}{3} \Omega$$

$$R_{12} = R_1 + R_2 \quad R_{1234} = \frac{10}{3} \Omega + 5 \Omega = \frac{25}{3} \Omega$$

$$\frac{1}{R_{eq}} = \frac{3}{25} + \frac{1}{5} = \frac{8}{25}$$

$$R_{eq} = \frac{25}{8} \Omega = 3.125 \Omega$$

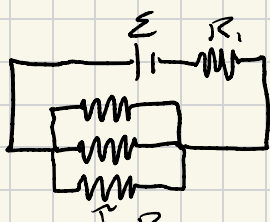29) $R_1 = 6 \Omega$ $R_2 = 18 \Omega$ $\varepsilon = 12V$



$$R_{eq} = R_1 + \frac{1}{\frac{1}{R_2} + \frac{1}{R_2} + \frac{1}{R_2}} \quad I = \frac{V}{R_{eq}}$$

$$R_{eq} = R_1 + \frac{R_2}{3}$$

$$R_{eq} = 6 \Omega + \frac{18 \Omega}{3}$$

$$R_{eq} = 12 \Omega$$

$$I_1 = \frac{I}{3}$$

$$I_1 = \frac{1}{3} A$$

a) $\frac{1}{3} A$

b) right


c) 720 J

$$W = \frac{J}{s} \quad t = 60s$$

$$P = IV = 1A \cdot 12V = 12W$$

$$12W \cdot 60s = 720J$$

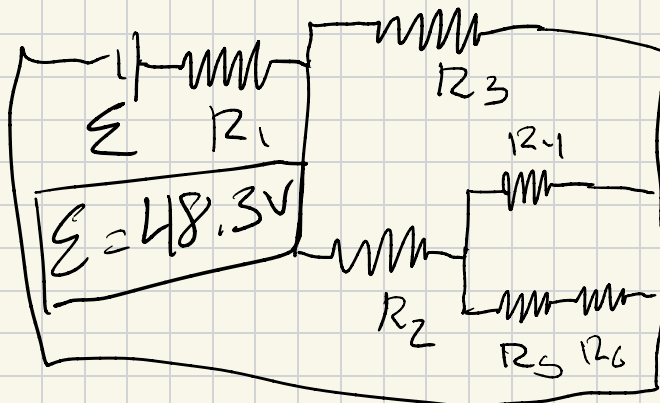33) $I_6 = 1.4A$ $R_1 = R_2 = R_3 = 2 \Omega$ $R_4 = 16 \Omega$ $R_5 = 8 \Omega$ $R_6 = 4 \Omega$ $I_S = I_6$



$$R_{eq} = R_1 + R_{23456} \quad V_6 = I_6 \cdot R_6$$

$$\frac{1}{R_{23456}} = \frac{1}{R_3} + \frac{1}{R_{456}}$$

$$R_{23456} = R_2 + R_{456}$$

$$\frac{1}{R_{456}} = \frac{1}{R_1} + \frac{1}{R_5}$$

$$R_{56} = R_5 + R_6$$

$$R_{56} = 12 \Omega$$

$$R_{456} = 6.86 \Omega$$

$$R_{2456} = 8.86 \Omega$$

$$R_{23456} = 1.63 \Omega$$

$$R_{eq} = 3.63 \Omega$$

$$V_S = I_6 R_5 \quad V_6 = I_6 \cdot R_6 \quad V_6 = 1.4 \cdot 4 \quad V_6 = 5.6V \quad V_S = 11.2V$$

$$V_S + V_6 = V_4 \quad I_4 = \frac{V_4}{R_4} \quad I_4 = \frac{16.8V}{16 \Omega} \quad I_4 = 1.05A$$

$$I_2 = I_4 + I_6 \quad I_2 = 1.05A + 1.4A \quad I_2 = 2.45A$$

$$V_3 = V_2 + V_6 \quad V_3 = 4.9V + 5.6V \quad V_3 = 10.5V$$

$$V_{tot} = V_1 + V_3 \quad V_{tot} = 26.6V + 21.7V \quad V_{tot} = 48.3V$$

58) $\mathcal{E} = 12V$ $R = 1.4M\Omega$ $C = 1.8\mu F$ $q_{end} = 16\mu C$

$$\tau = R \cdot C$$

$$\tau = 1.4M\Omega \cdot 1.8\mu F = 2.52s$$

$$Q = \mathcal{E} \cdot C$$

$$Q = 12V \cdot 1.8\mu F = 21.6\mu C$$

$$q_{end} = Q(1 - e^{-t/\tau}) \quad 16\mu C = 21.6\mu C(1 - e^{-t/2.52})$$

$$0.74 = 1 - e^{-t/2.52}$$

$$e^{-t/2.52} = 0.259$$

$$\frac{-t}{2.52} = \ln(0.259)$$

$$-t = 2.52 \ln(0.259)$$

$$t = 3.4 \text{ seconds}$$

a) $\tau = 2.52 \text{ sec}$
 b) $Q = 21.6\mu C$
 c) 3.4 sec

64) $V = 100V$

$$V = V_0 e^{-t/\tau} \quad V_{17} = 100V e^{-\frac{173}{2.175}}$$

$$V = 100V e^{-\frac{10}{\tau}} \quad V_{17} = 39.6mV$$

$$\frac{1}{100} = e^{-\frac{10}{\tau}}$$

$$\ln\left(\frac{1}{100}\right) = -\frac{10}{\tau}$$

$$R_C = \frac{-10s}{\ln\left(\frac{1}{100}\right)}$$

$$R_C = 2.17 \text{ sec}$$

a) $2.17 \text{ sec} = \tau$
 b) $39.6mV = V_{17}$